

MA5: Control a robot (sensors + motor + transistors)


Emil Joakim Jensen Bartholdy (emba), Alexander Oliver (alol) & Alma Rosager Freiesleben (alfr)

Date: 10-03-2021


Basic Sensor Circuits

- Control LED intensity with a potentiometer

This is our BB:

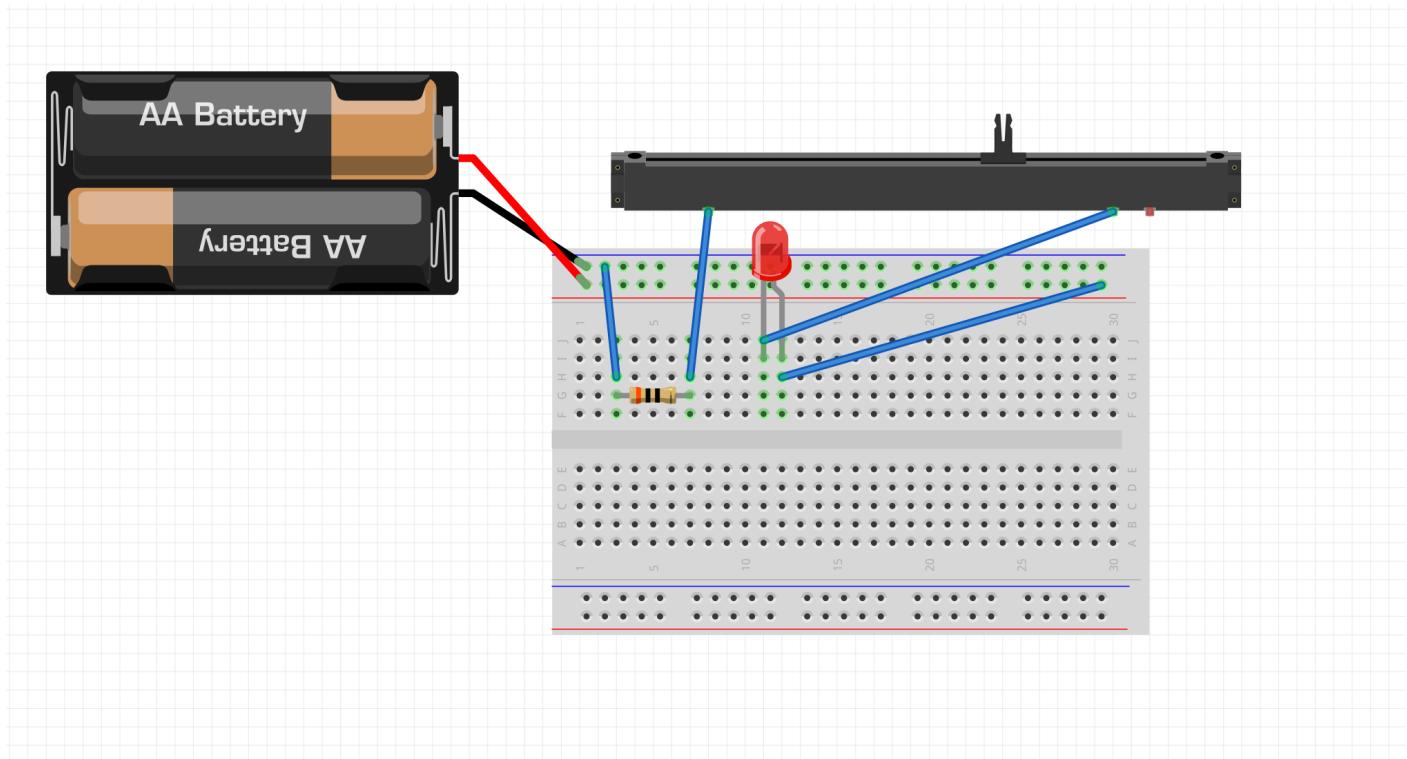


This is our SCH:

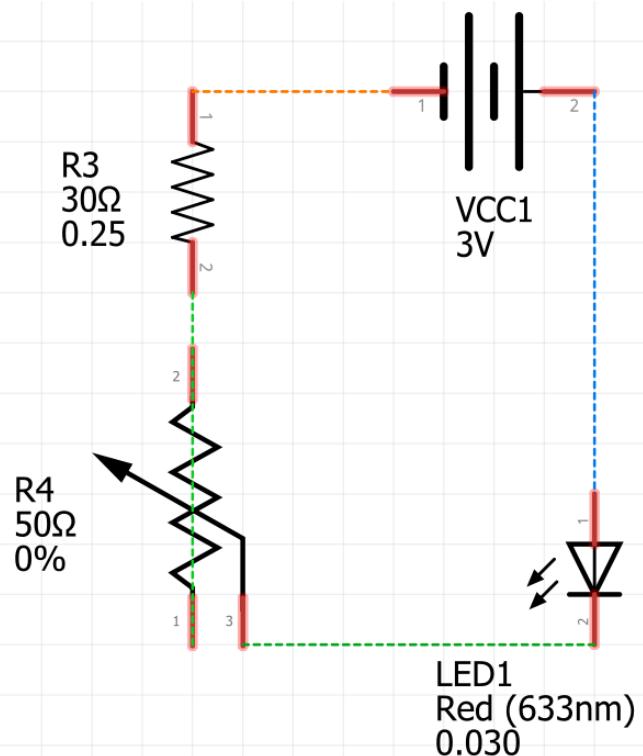


- Read a potentiometer

This is our BB:

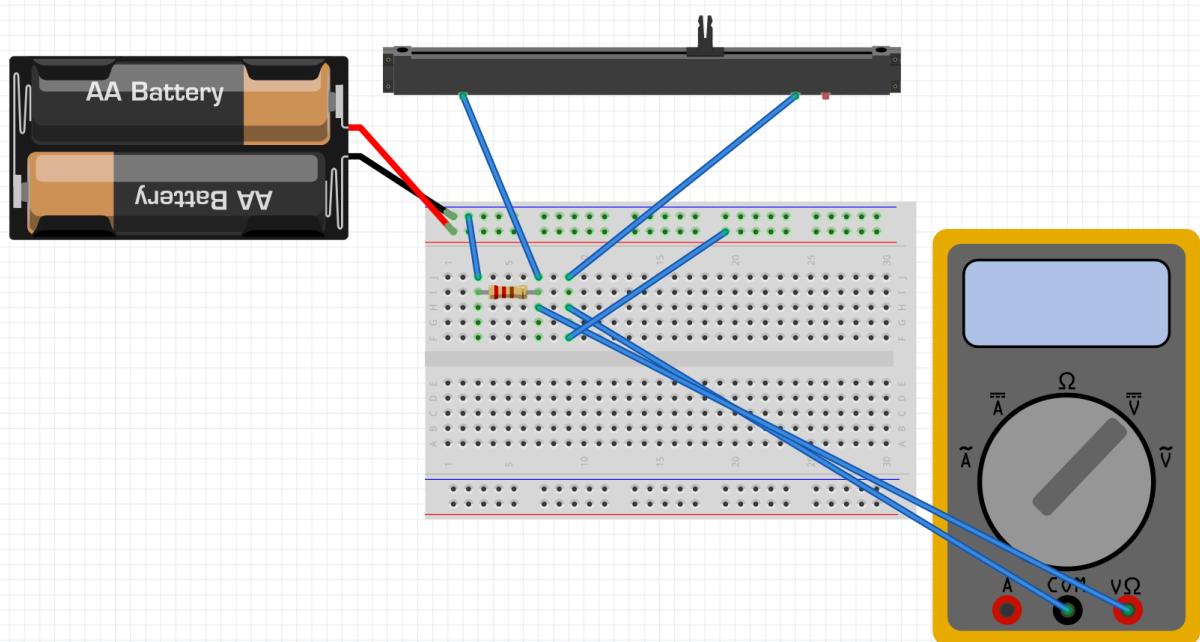


This is our SCH:

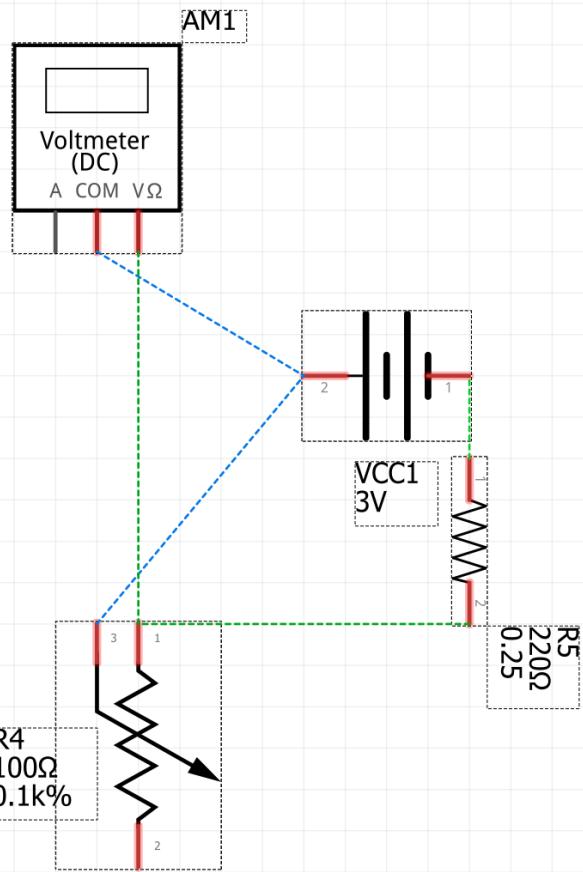


- Read the status of a switch with a multimeter

This is our BB:

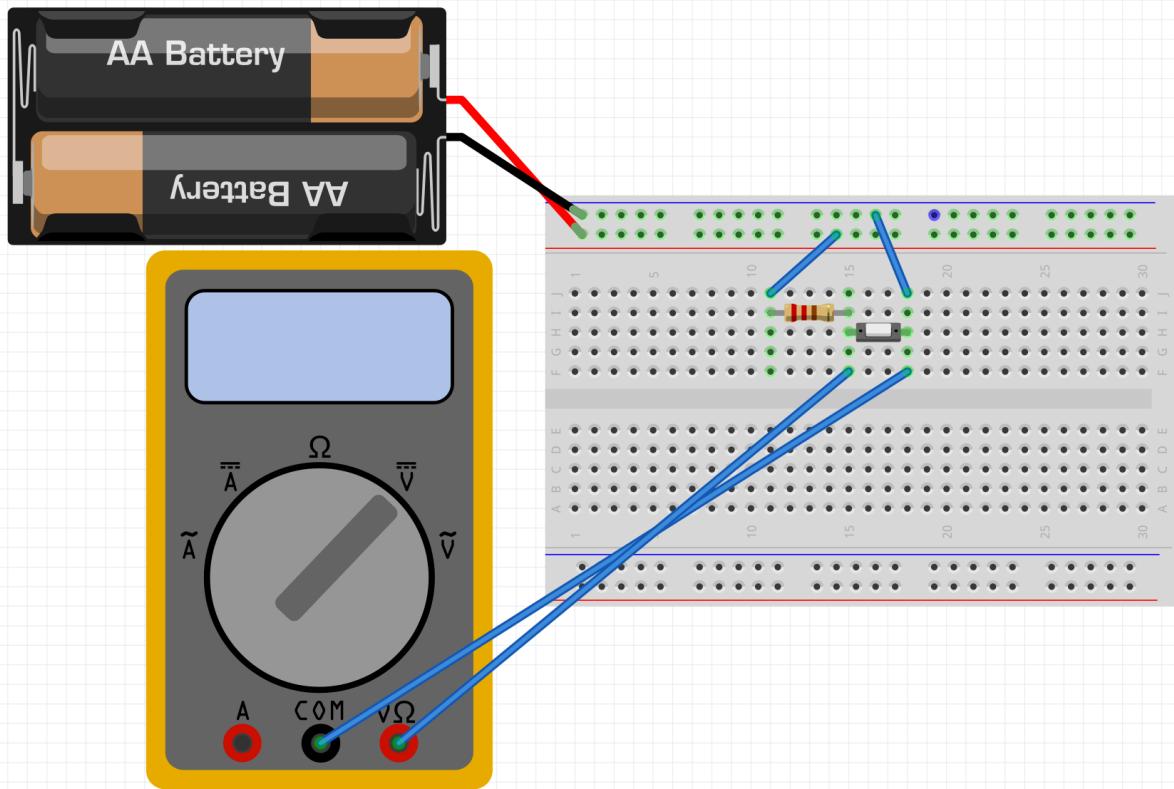

61


This is or SCH:

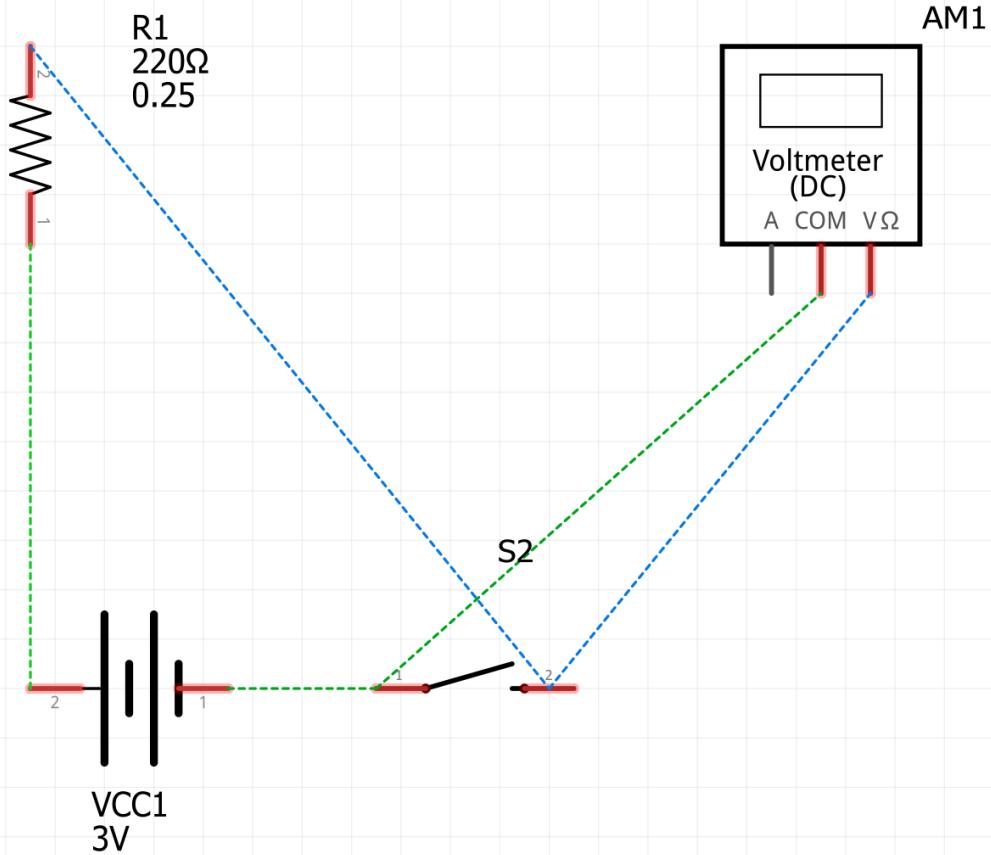


Robot Controlling Circuits

- A circuit to test a digital IR sensor FC-51

This is our BB:

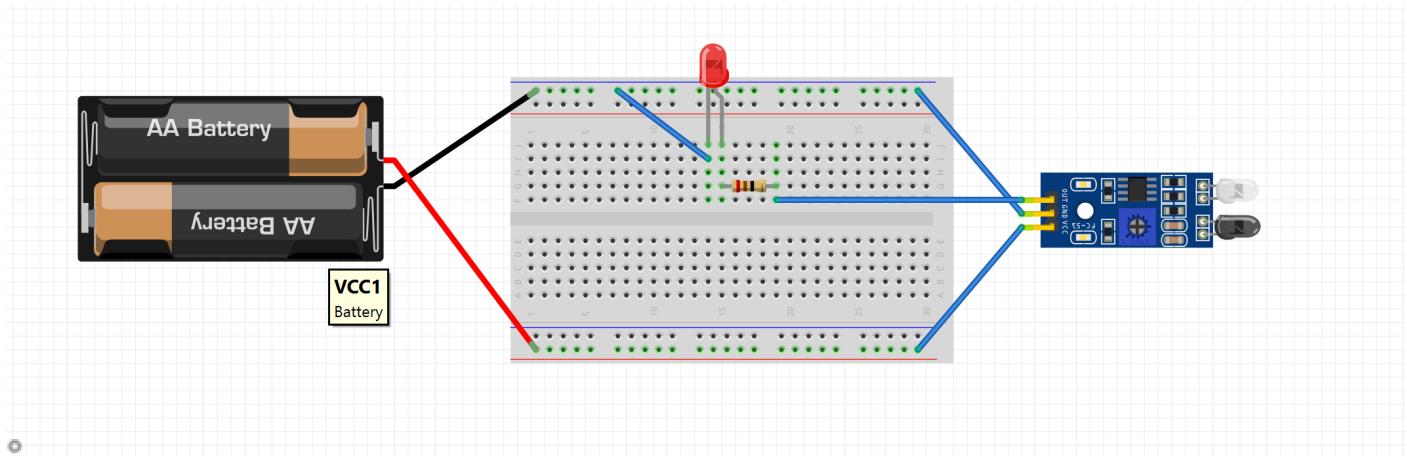


This is our Schematic:

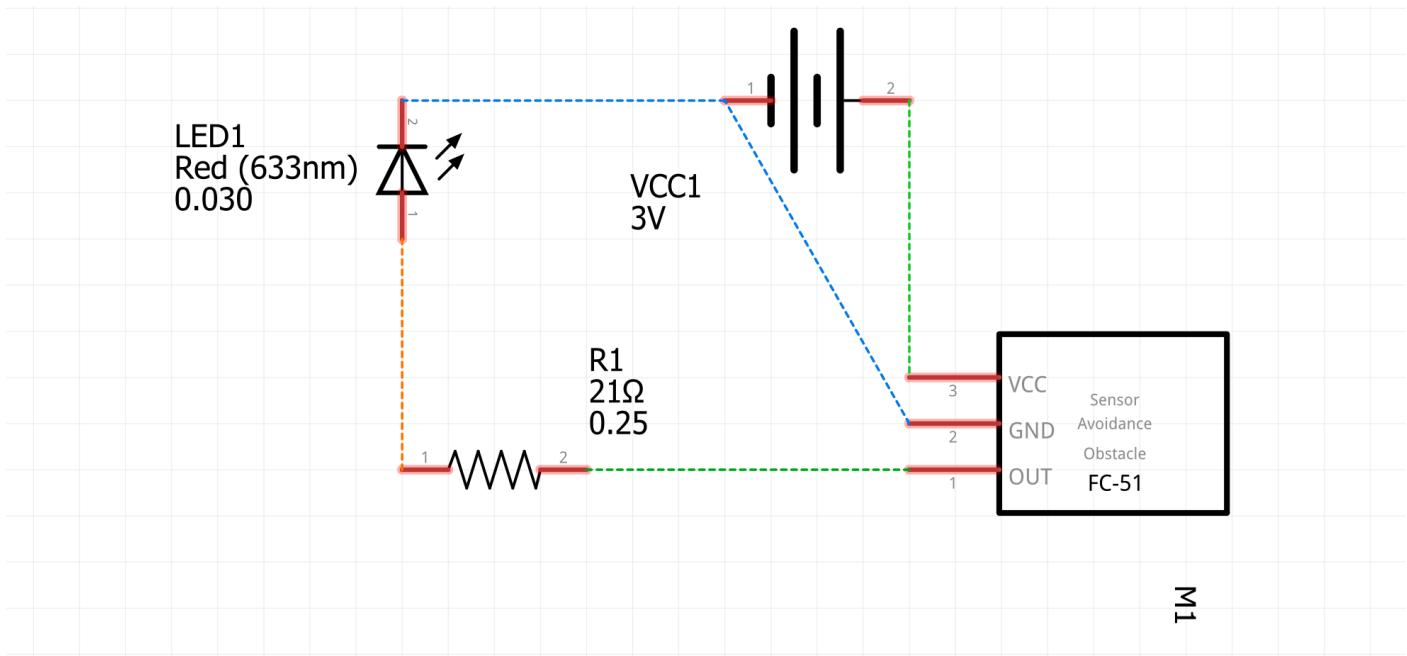


- A circuit to test an analogue IR sensor

This is our BB:

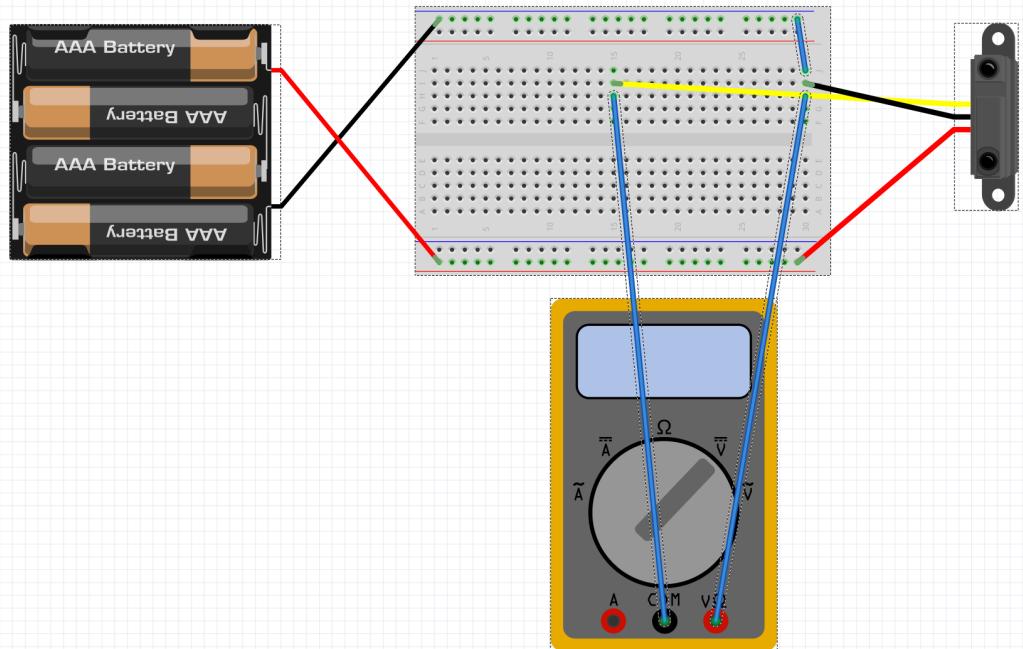


1 - 0 - ~

This is our SCH:

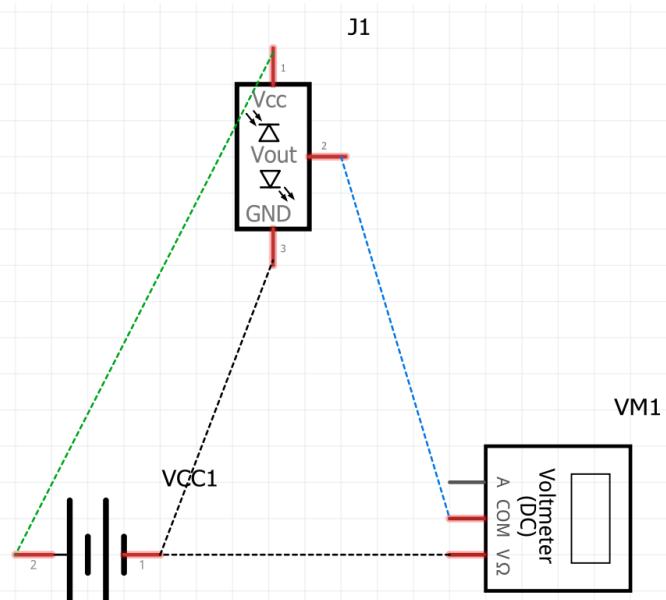


- An H-bridge with switches and control a motor

This is our BB:

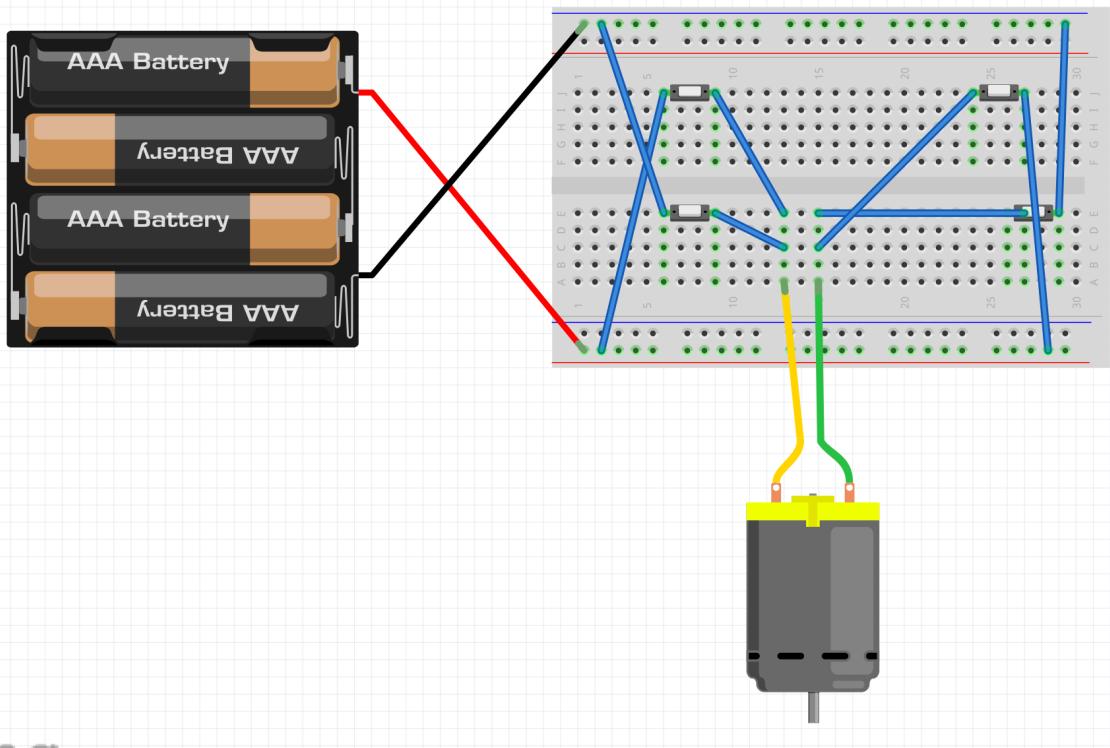


This is or SCH:

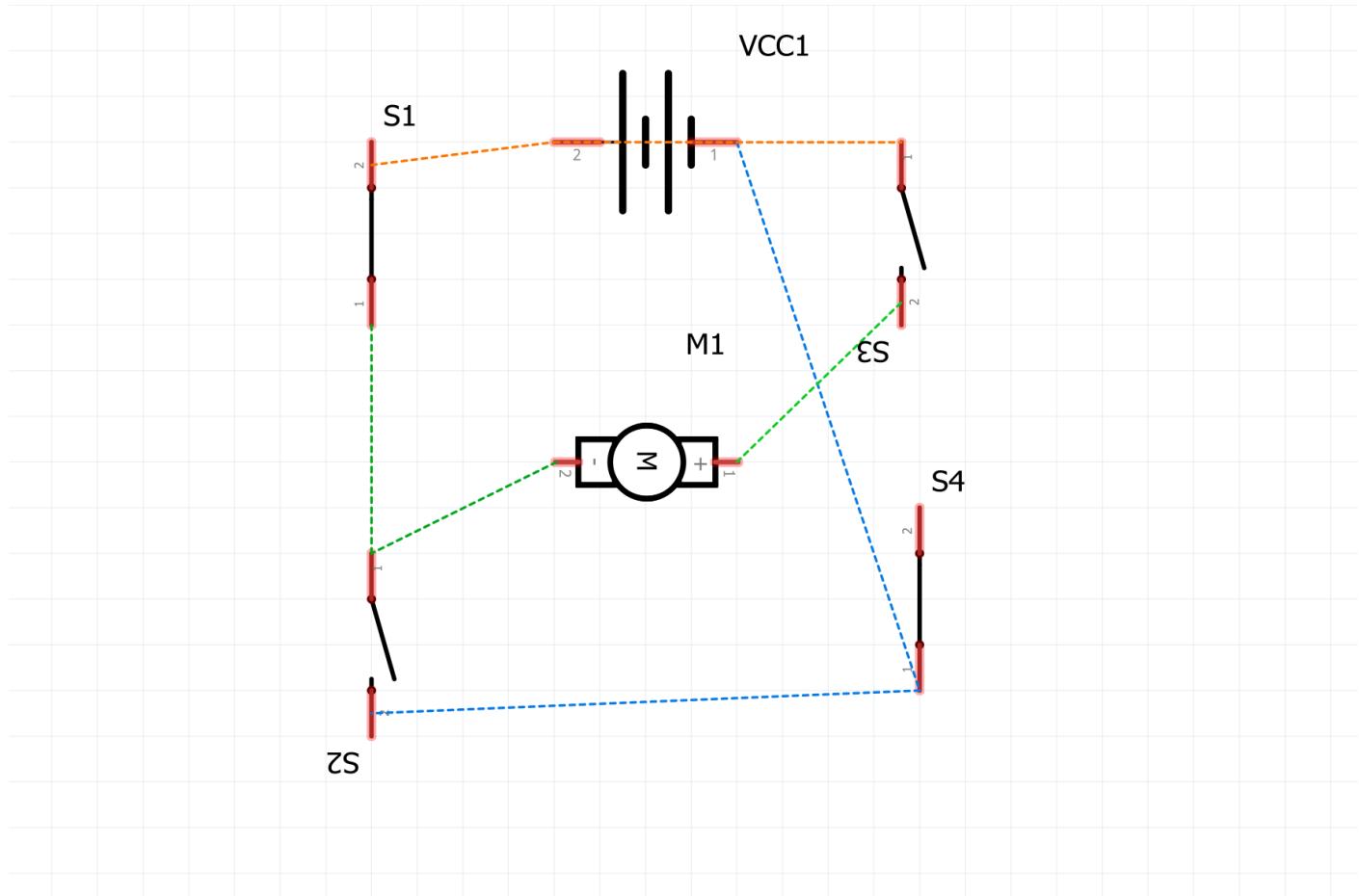

Questions and misunderstandings

We had a hard time with Fritzing, mostly with applying OHMs law and calculate the different parameters of the formula.

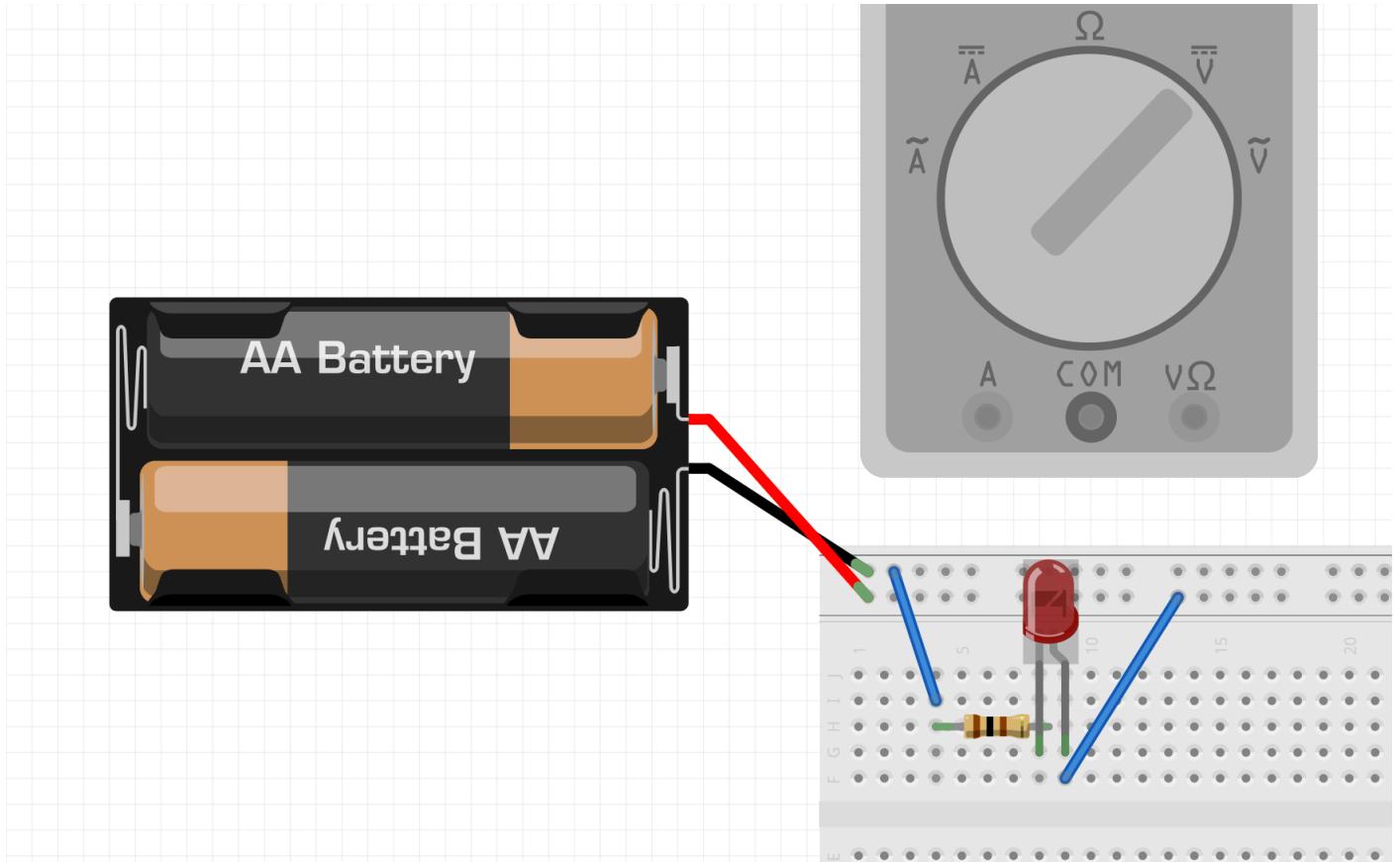1. How does a multimeter measure drop in resistance (slide 050-18)?
2. Why does red led not light up with circuit current of 30mA?



3. In circuit #4: why does it draw more current when the IR sensor does not detect anything, and less when it does?

